



Train Detection



And Simple Signaling



By Scott Russell 01/11/14

Simplest Train Detection

Train




John



“I see there is a train in that block”

Turnout Position Indication

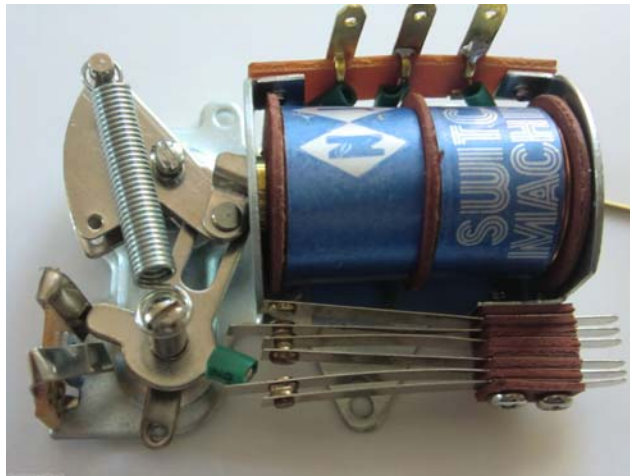- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)



Turnout Position Indication

- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)
 - Tortoise switch machine contacts (sliding style)



Turnout Position Indication

- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)
 - Tortoise switch machine contacts (sliding style)
 - Atlas switch machine contacts (sliding style)



Turnout Position Indication

- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)
 - Tortoise switch machine contacts (sliding style)
 - Atlas switch machine contacts (sliding style)
 - Hand throws with contacts



Turnout Position Indication

- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)
 - Tortoise switch machine contacts (sliding style)
 - Atlas switch machine contacts (sliding style)
 - Hand throws with contacts
 - Electrical or mechanical switches/relays separately actuated




Turnout Position Indication


- Detection: Need to know which way the turnout is thrown
 - Auxiliary Contacts – What is needed depends on the signal circuit
 - Solenoid switch machine contacts (relay style)
 - Tortoise switch machine contacts (sliding style)
 - Atlas switch machine contacts (sliding style)
 - Hand throws with contacts
 - Electrical or mechanical switches/relays separately actuated
- Indication: What to do now that you know the turnout position
 - Single Color LED's or bulbs
 - Bi-color (Bi-polar) LED's
 - 2 lead
 - 3 lead

Signal or Panel Indication

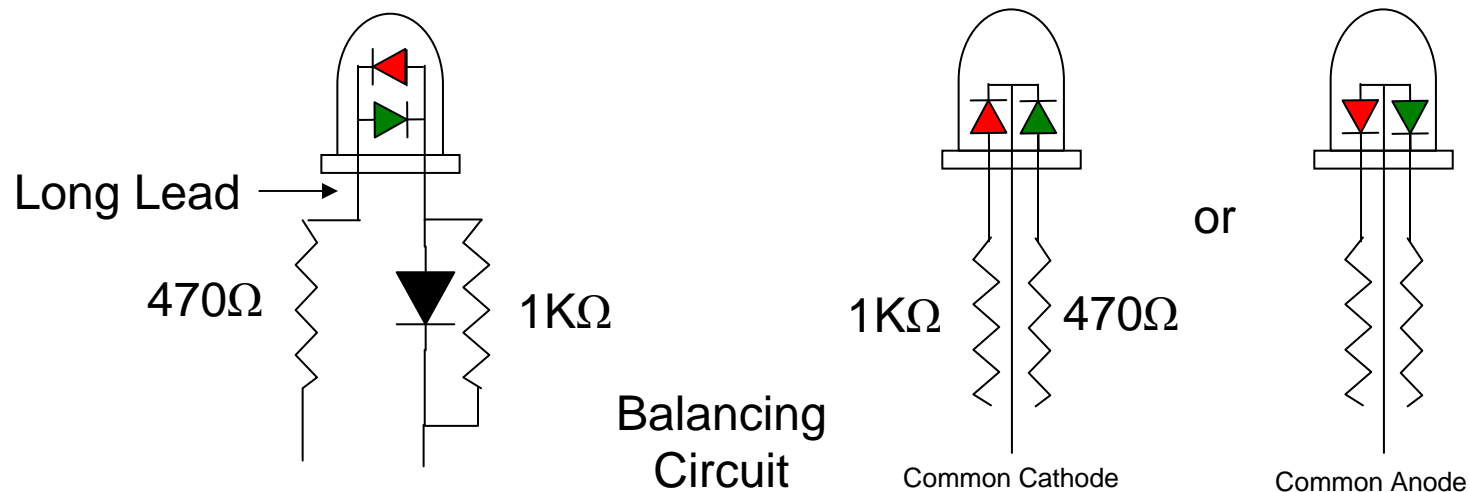- Doesn't matter where you put the signal (panel or layout, or both)
- A bulb is a voltage device – rated voltage or slightly lower
- An LED is a current device – voltage only has to be high enough to turn it on, but can be much higher. Resistor controls the current.
- A Bi-color LED can indicate yellow if both red and green are on at the same time (requires AC on 2-lead device)




Tortoise Panel Indicator Circuit

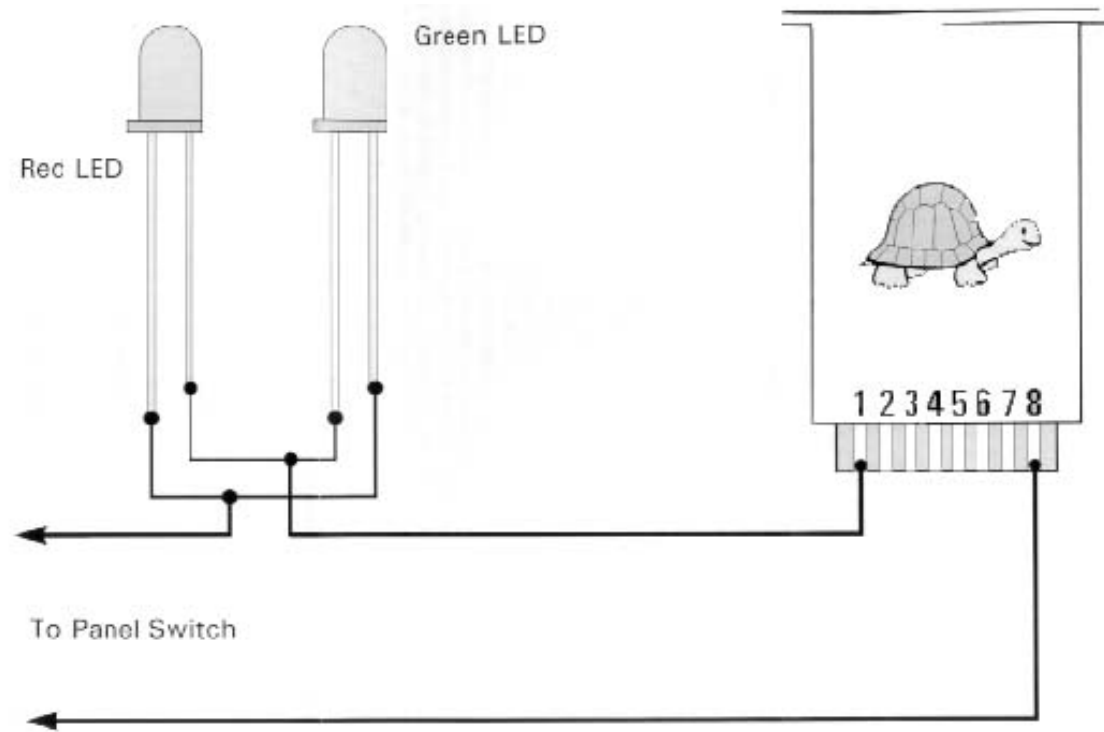

<http://www.tonystrains.com/technews/archive/circuitron.htm>


Tortoise Signal/Turnout Circuit

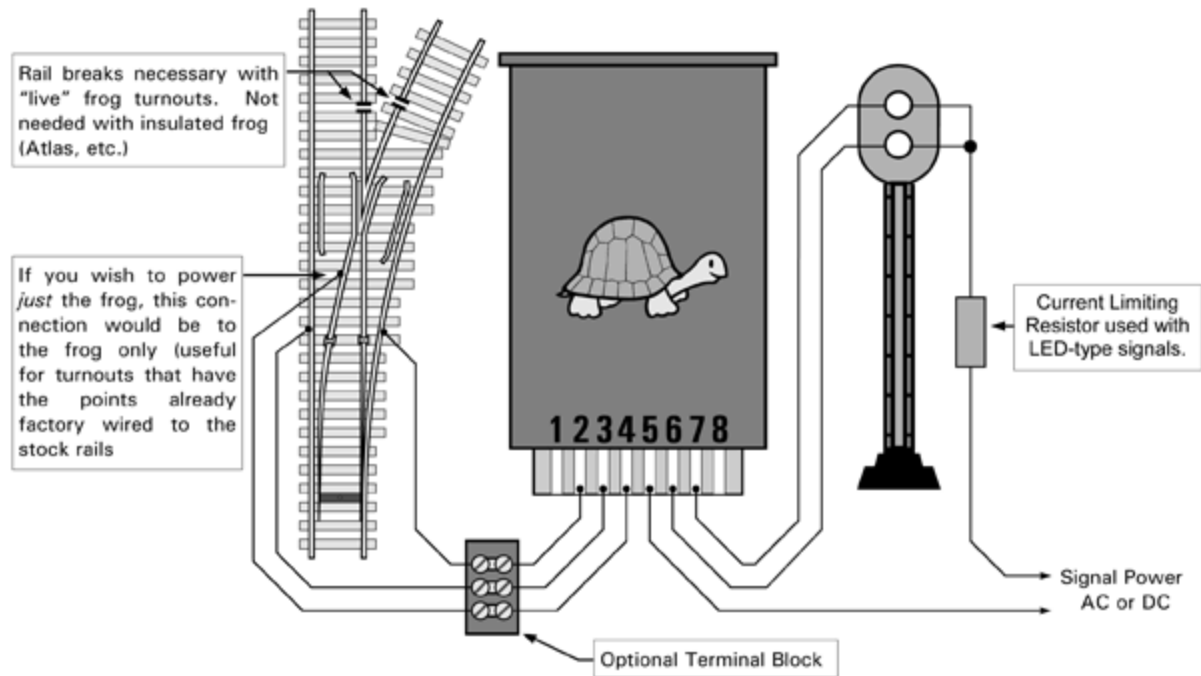

<http://www.tonystrains.com/technews/tortoise/signal-wiring.htm>


Typical Signal Indication

Depends on your prototype, or preference

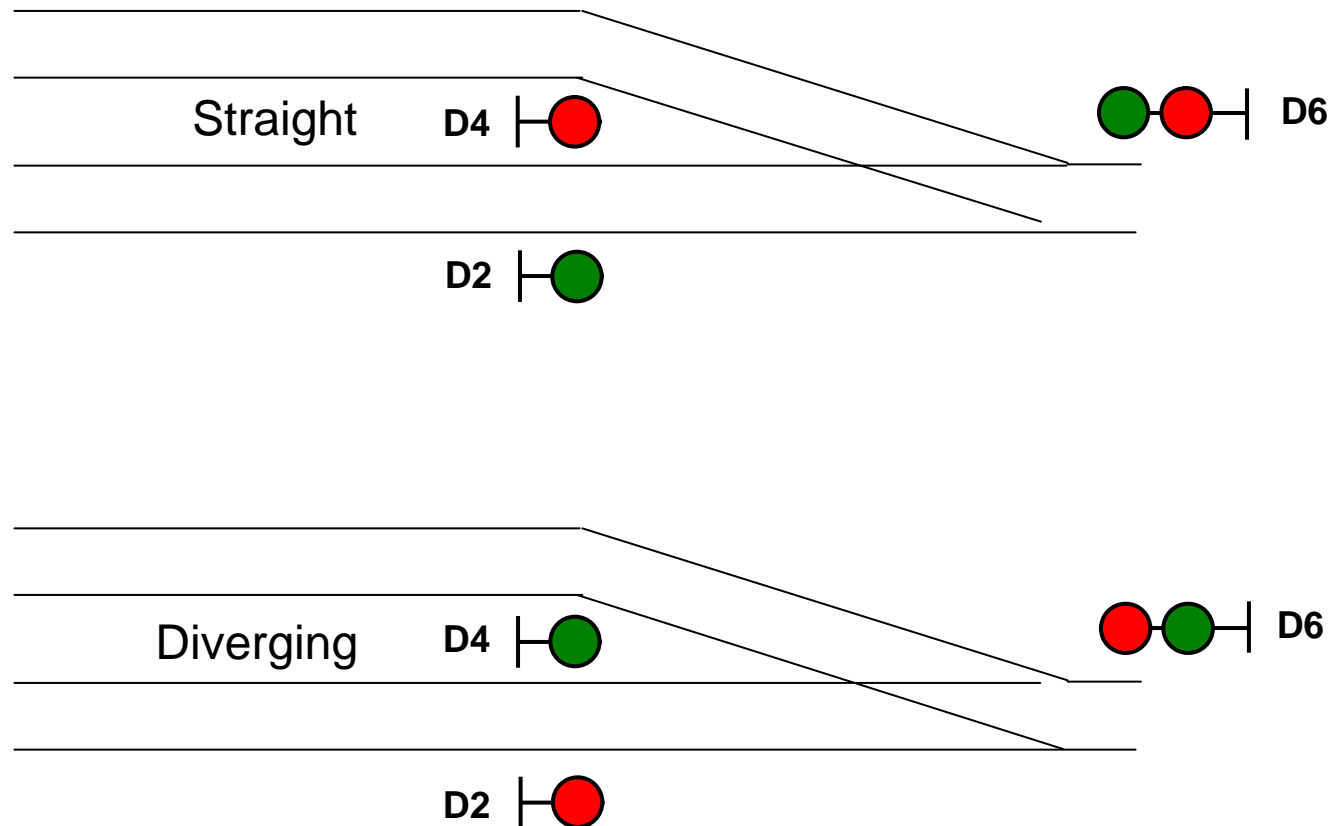

Dwarf Signal Circuit for Turnout

3 Lead LED's

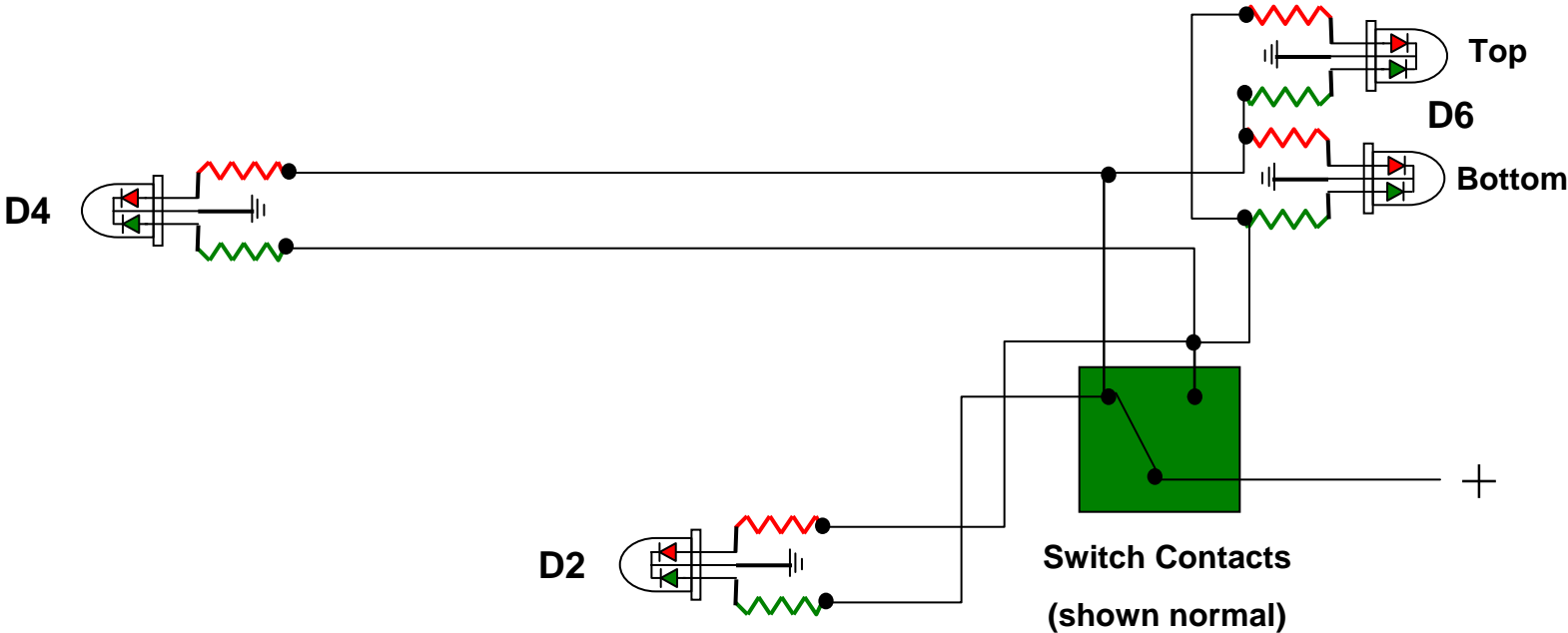


Normal = D2 Green; D6 = Top Green, Bottom Red; D4 = Red

Reversed = D2 Red; D6 = Top Red, Bottom Green; D4 = Green

Dwarf Signal Circuit for Turnout


2 Lead LED's

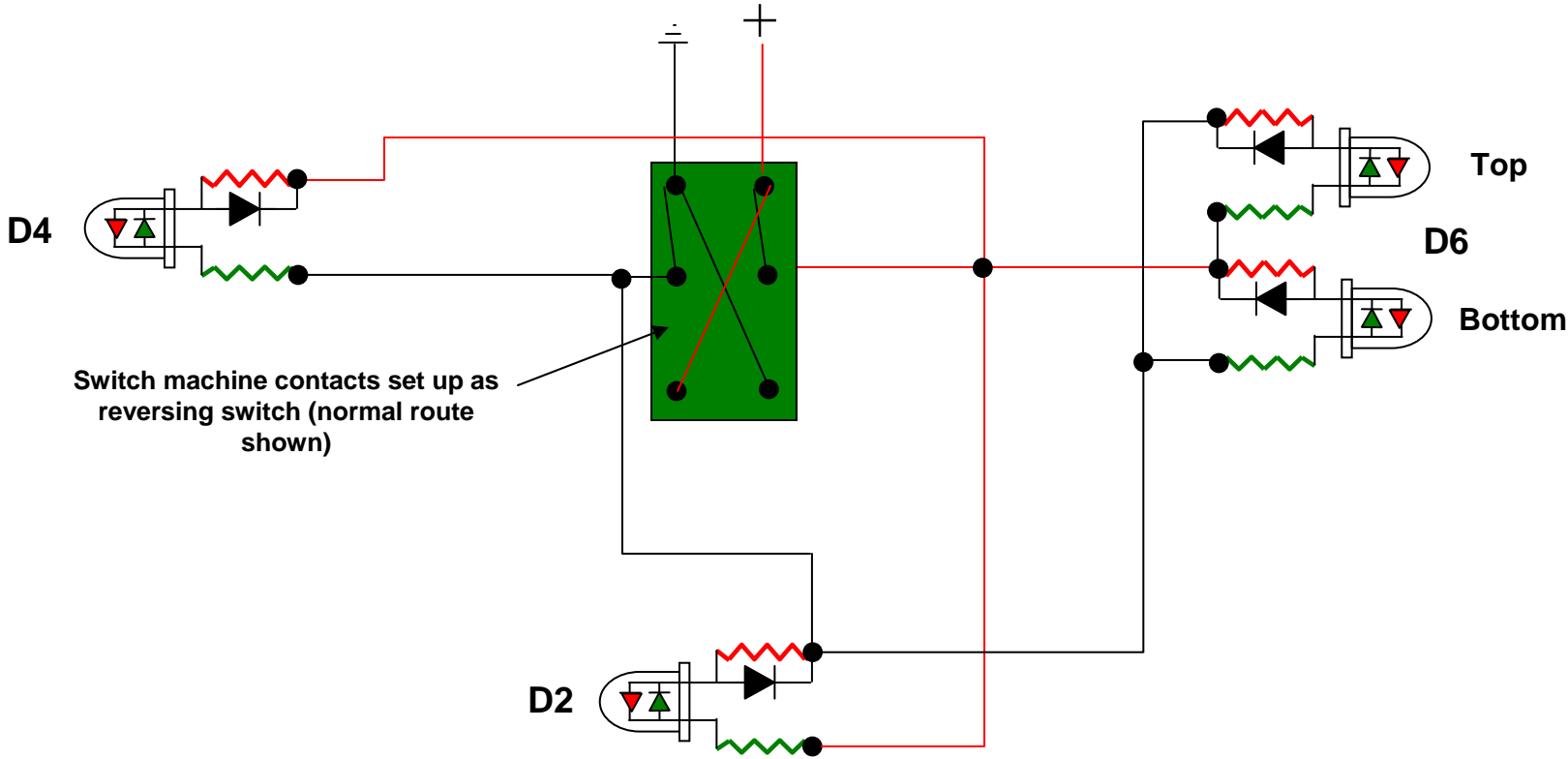

Straight: D2 = Green; D6 = Top Green, Bottom Red; D4 = Red


Diverging: D2 = Red; D6 = Top Red, Bottom Green; D4 = Green

Maybrook / Seaview Ave Signals

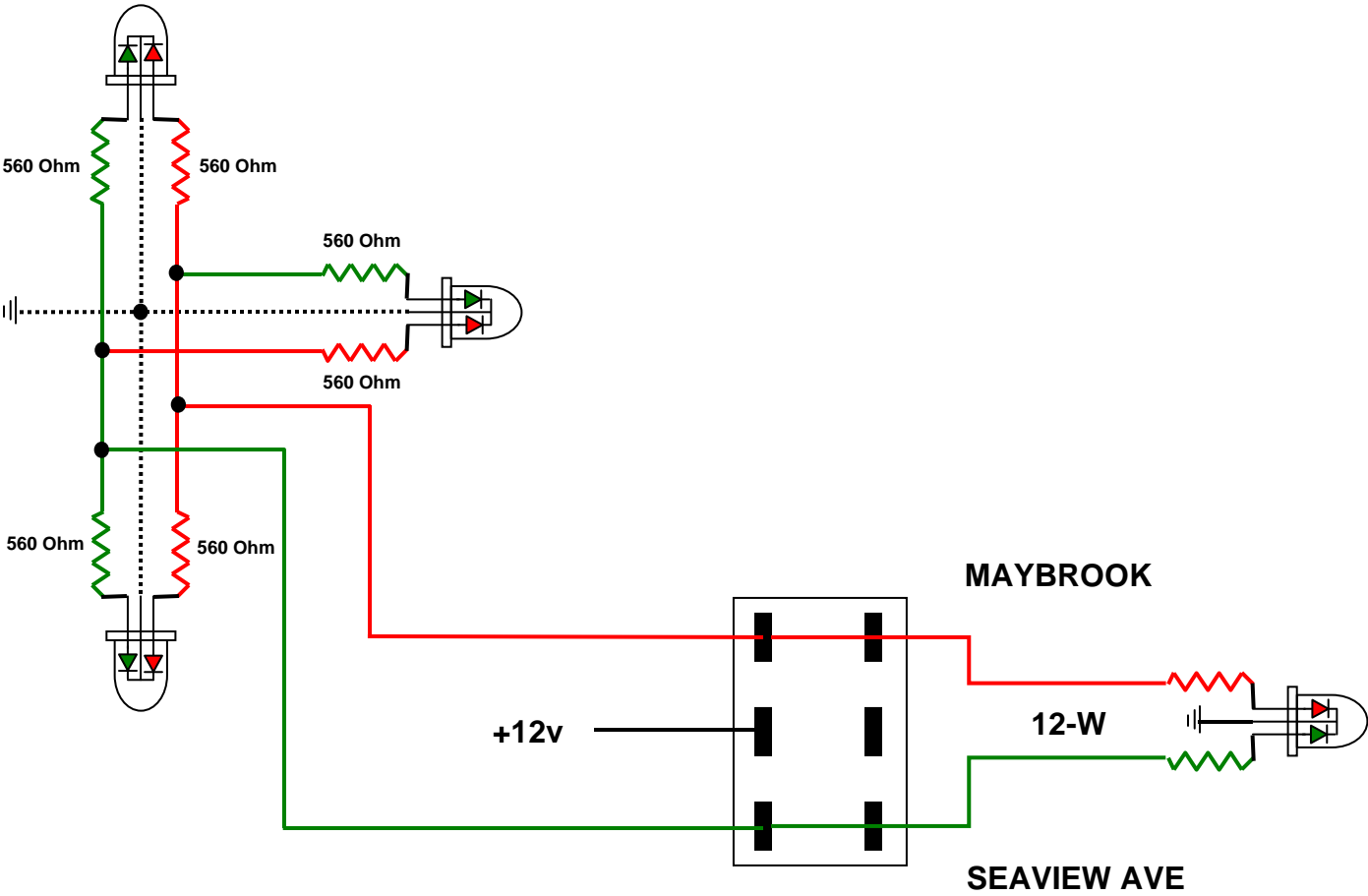

Turnout Indication with Separate Relay

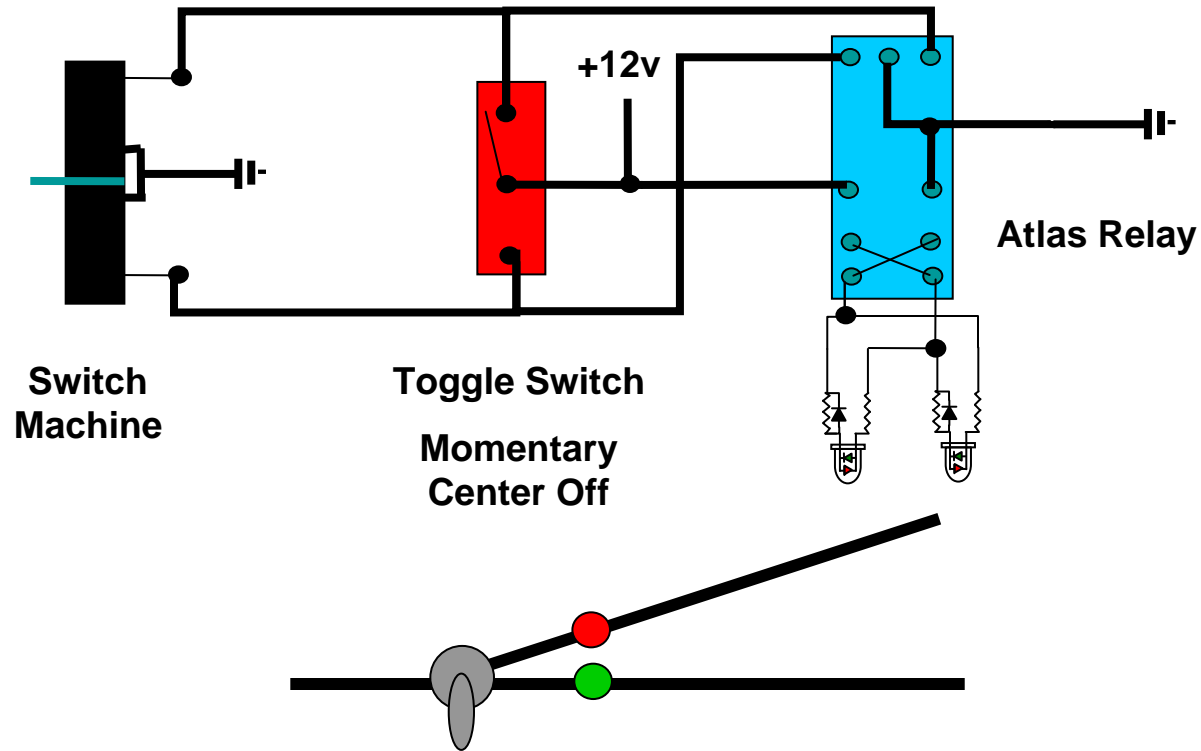Switch Panel w/Bi-Color LED Indicators
(1 turnout shown)



Block/Train Detection

- Basic detectors: Non-contact, not part of track circuit
 - Components
 - Photocells (CdS, CdSe)
 - Phototransistors / Photodarlingtons (Silicon)
 - Photo Schmitt Detectors (Silicon)
 - Reflective
 - Magnetic (reed switch, Hall Effect)
 - “Store Bought”
 - Dallee Trak-DT (current sensing), Opto-DT (IR)
 - Circuitron DT-1,2,3,4 (uses Photocells)

Basic Detectors

Components



CdS / CdSe



TO-46c



T1 (3mm)




Sidelooker



Phototransistors / Photodarlington




Sidelooker
PhotoSchmitt

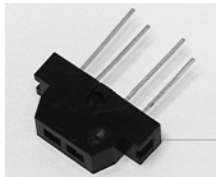

Reflective

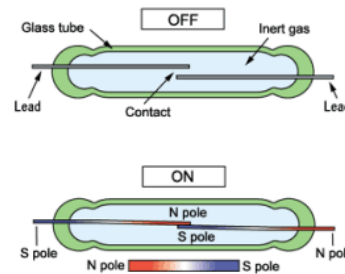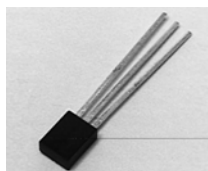

Reed Switch

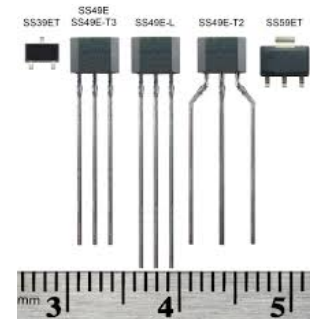


Hall Effect Sensor

Basic Detectors

“Store Bought”



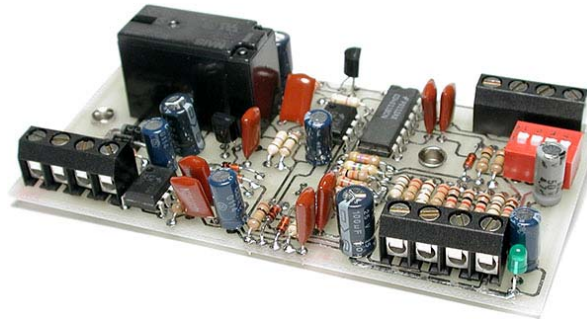
Shameless Plug for John Grosner's Photocell Circuit




Dallee Opto-DT




Dallee Trak-DT

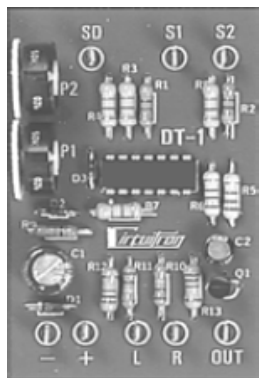

DT-1 Grade Crossing Detector

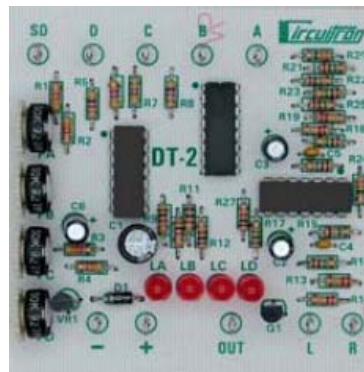


DT-2 Grade Crossing Detector
w/Logic

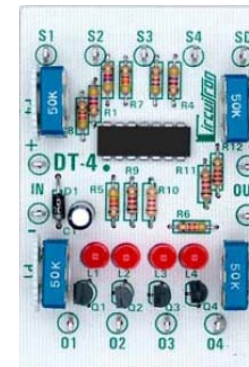

DT-4 Rolling Stock Detector

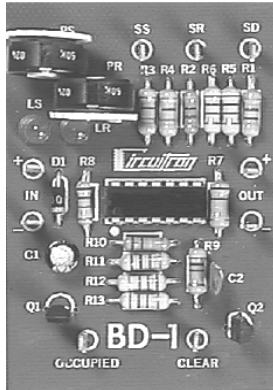
More Sophisticated Detectors and Signaling Topics for next Clinic



Circuitron BD-1




Digitrax BD-4

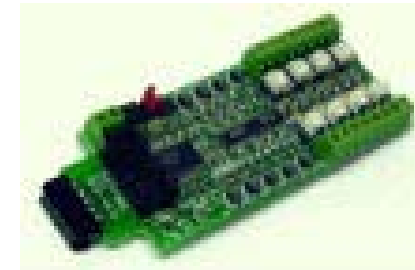

RR-CirKits BOD-8



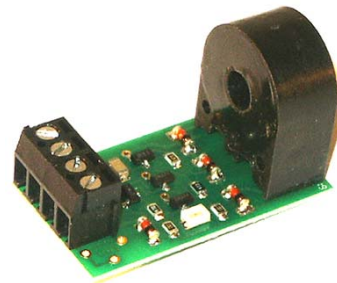Integrated Signal
Systems
Block Occupancy
Detector



NCE BD-20



DCC Specialties
Block Watcher

Block 4 & 12 Detection for Diamond Interlocking and Semaphore Signal

